

Analog VLSI Circuit Final Project

Presented By-

Group-4

Akash Ganguly – SC18B072

Kothadiya Prince - SC18B078

Kshitij Singh – SC18B079

Aditya Amrit – SC18B087

Vivek Garg – SC18B093

Contents

- Objective
 - Design Requirement
- Current Mirror Network
 - Cascode pair biasing
- Folded Cascode Design
 - Design Calculation
 - NMOS-PMOS-Overall Design
 - Results
- CMFB
 - Design
 - Buffer Design
 - Results & Analysis
- 2nd Stage Design
 - Design Calculation
 - Results
- Final Results & Conclusion
- References


Objective

Design Requirements

- $A_v \geq 70 \text{ dB}$
- $UGF \geq 100 \text{ MHz}$
- Fully Differential OpAmp
- Rail-to-Rail input capability
- CMFB
- $C_L = 500 \text{ fF}$

Current Mirror


Current Mirror

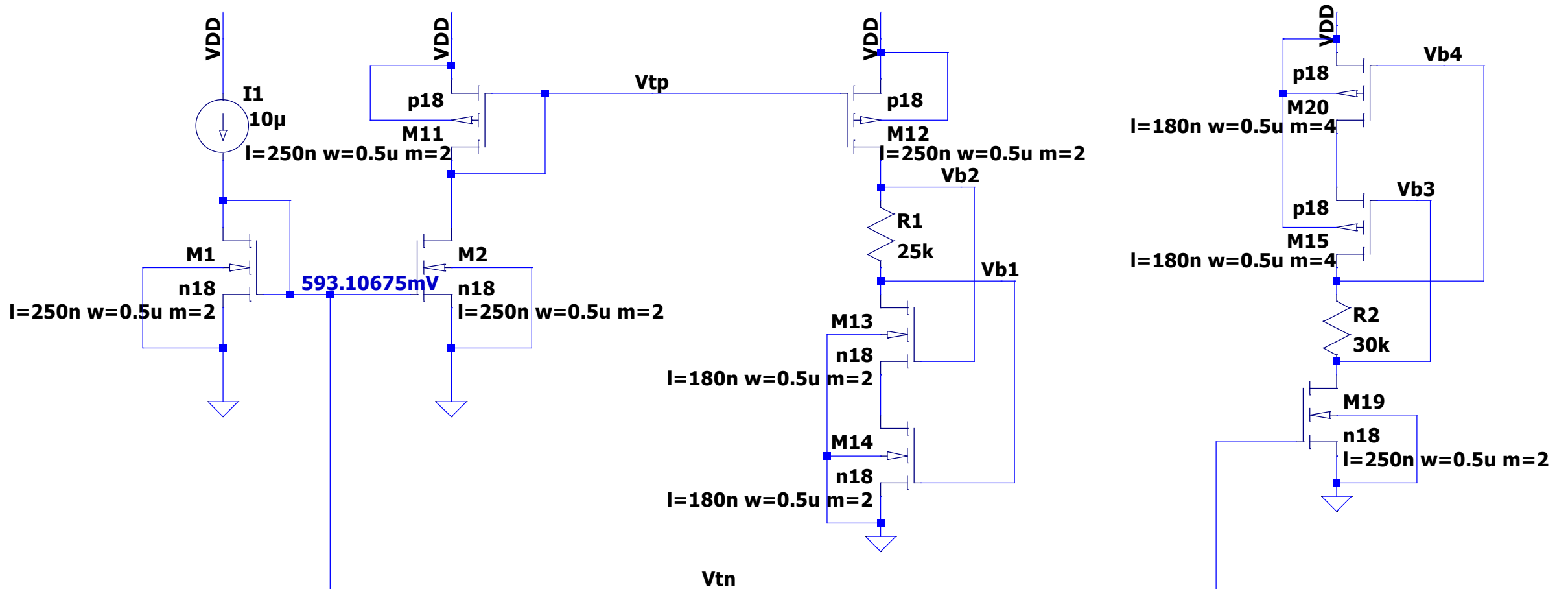

Current Mirror

- V_{tp} – biases PMOS Tail Current for M0p Transistor
- V_{tn} – biases NMOS Tail Current for M0n Transistor and others
- V_{b1} – biases M3 and M4 Transistor(Lower NMOS Stack)
- V_{b2} – biases M5 and M6 Transistor(Upper NMOS Stack)
- V_{b3} – biases M7 and M8 Transistor(Lower PMOS Stack)
- V_{b4} – biases M9 and M10 Transistor(Upper PMOS Stack)

Current Mirror

 


Folded Cascode Rail-to-Rail Design

Design Budgeting

- $UGF \approx \frac{g_m}{2\pi C_L} \geq 100\text{MHz}$
- $\Rightarrow g_m \geq 2\pi \times 100\text{MHz} \times C_L$
- $\Rightarrow g_m \geq 0.314\text{mS}$

- Let's choose $g_m = 1\text{ mS}$
- Let the design $V_{in,cm} = 0.9\text{V}$
- $0.6\text{V} - V_{gs}$ biasing
- $0.3\text{V} - V_{dssat}$ + margin for tail current source

NMOS Characterization

 


Id:	1.13e-05
Vgs:	6.00e-01
Vds:	3.00e-01
Vbs:	0.00e+00
Vth:	4.82e-01
Vdsat:	1.30e-01
Gm:	1.34e-04

We must scale NMOS such that $g_m = 1\text{mS}$

$$W_{\text{req.d}} = 7.4 * W_1$$

PMOS Characterization

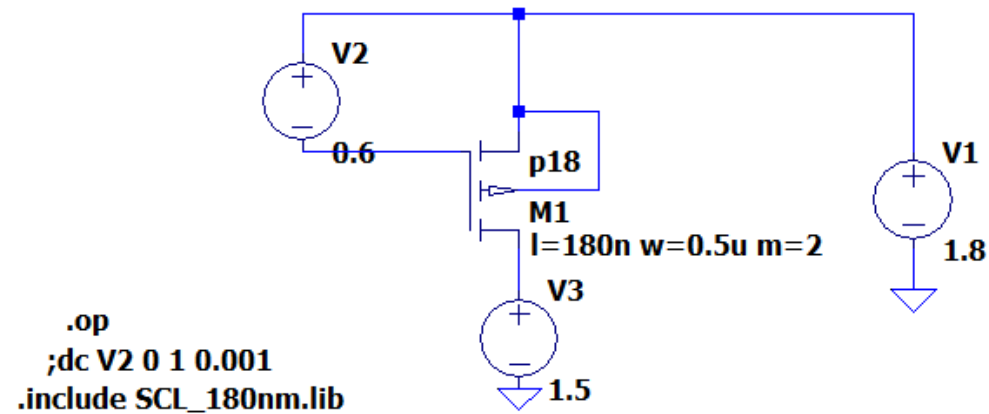


Id:	1.62e-06
Vgs:	6.00e-01
Vds:	3.00e-01
Vbs:	0.00e+00
Vth:	5.16e-01
Vdsat:	9.91e-02
Gm:	2.35e-05

We must scale PMOS such that $g_m = 1\text{mS}$

$$W_{\text{reqd}} = 42.5 * W_1$$


NMOS Input Pair

• Name:	m1n	m2n	m0n
• Model:	n18	n18	n18
• Id:	7.39e-05	7.39e-05	1.48e-04
• Vgs:	6.17e-01	6.17e-01	5.93e-01
• Vds:	1.27e+00	1.27e+00	2.83e-01
• Vbs:	-2.83e-01	-2.83e-01	0.00e+00
• Vth:	5.30e-01	5.30e-01	4.63e-01
• Vdsat:	1.12e-01	1.12e-01	1.42e-01
• Gm:	9.75e-04	9.75e-04	1.69e-03
• Gds:	1.99e-05	1.99e-05	5.83e-05

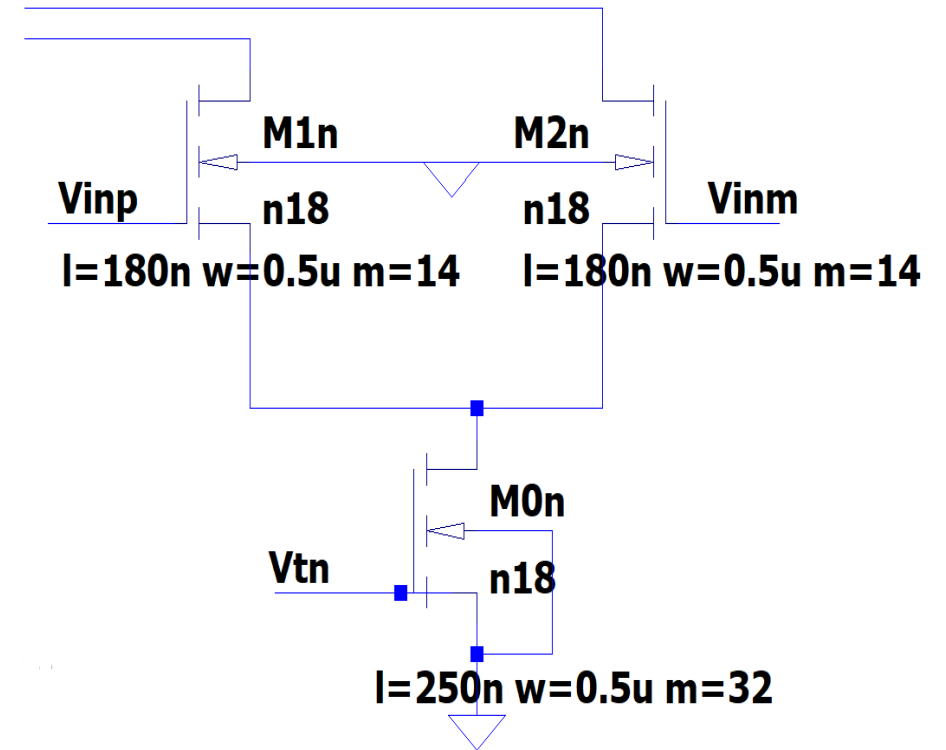


PMOS Input Pair

• Name:	m1p	m2p	m0p
• Model:	p18	p18	p18
• Id:	-6.30e-05	-6.30e-05	-1.26e-04
• Vgs:	-6.47e-01	-6.47e-01	-7.17e-01
• Vds:	-1.30e+00	-1.30e+00	-2.53e-01
• Vbs:	2.53e-01	2.53e-01	0.00e+00
• Vth:	-5.30e-01	-5.86e-01	-4.32e-01
• Vdsat:	-9.10e-02	-9.10e-02	-2.42e-01
• Gm:	9.77e-04	9.77e-04	7.37e-04
• Gds:	1.67e-05	1.67e-05	1.06e-04

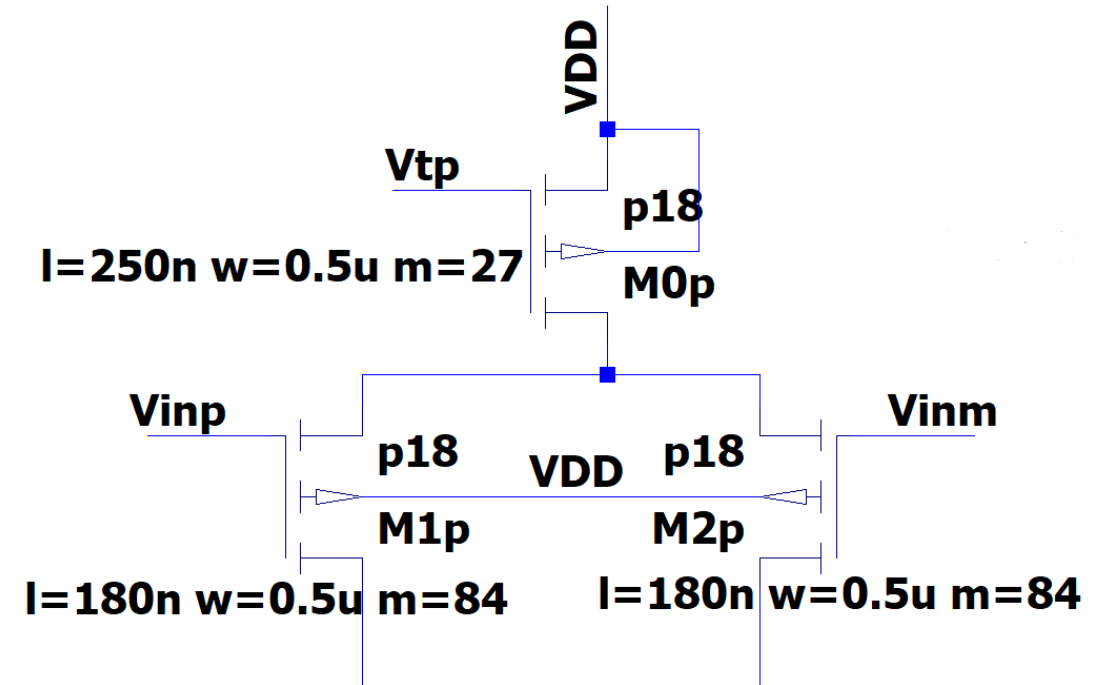


Main Transistor Stack

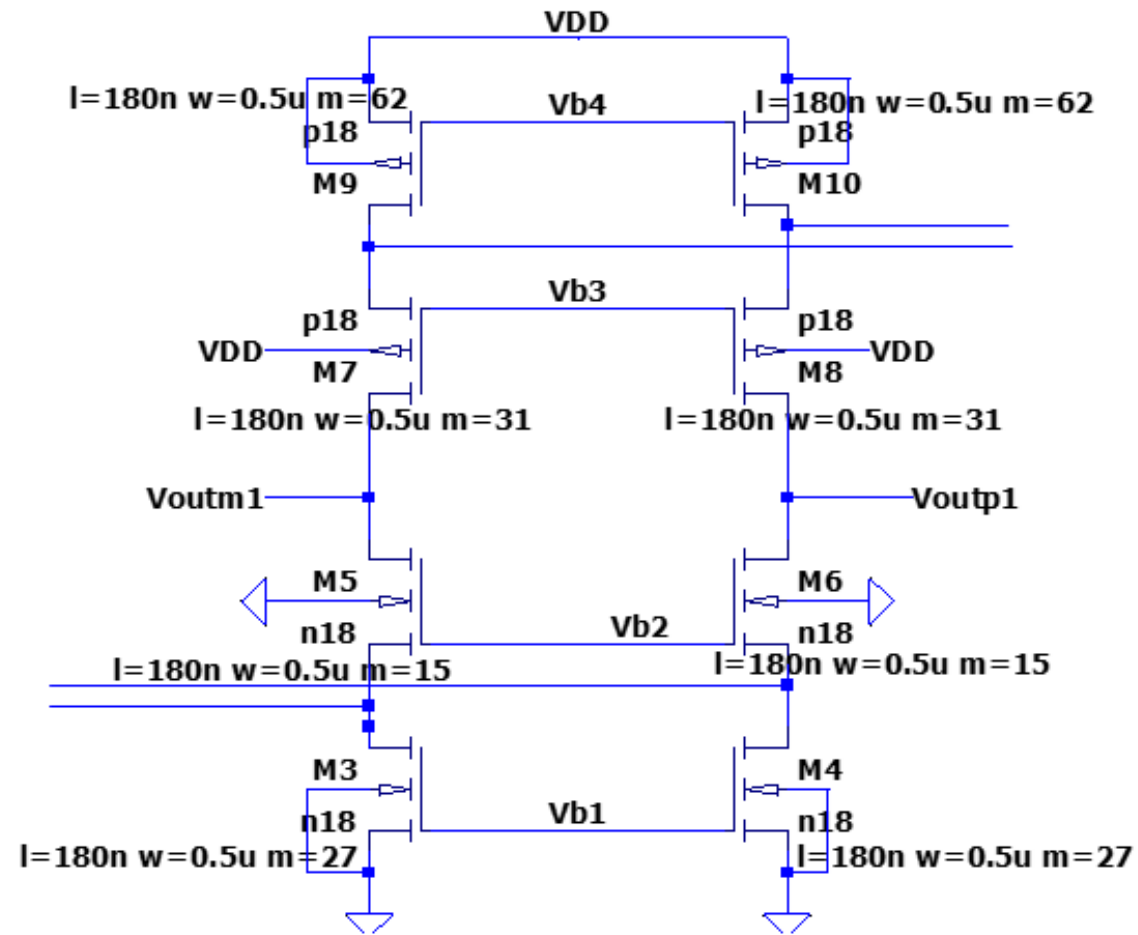

Main Transistor Stack


	M3	M5	M7	M9
I_D	149 μ A	86.1 μ A	86.1 μ A	160 μ A
V_{GS}	601mV	637mV	759mV	700mV
g_m	1.75mS	1.05mS	0.841mS	1.49mS
r_o	10.2k Ω	27.78k Ω	56.82k Ω	13.26k Ω

Circuit Design

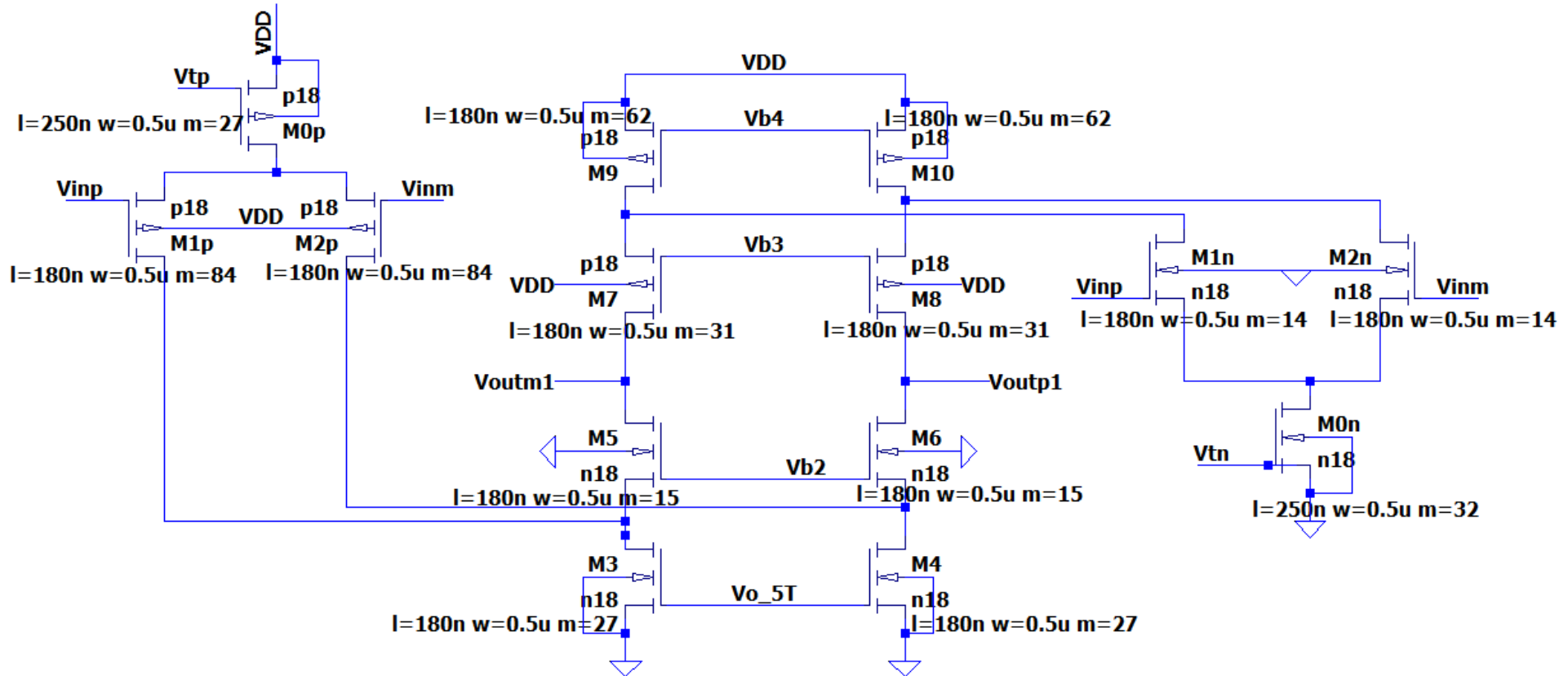


NMOS-PMOS Folded Cascode design

DC Analysis

 


- Input CM Voltage
 - Sweep from -0.5V to 2.5V
- Output DC Voltage
 - Range: 0.7V to 1V
- Rail to Rail working capability
 - Input CM voltage
 - 0.7V to 1V

AC Analysis($V_{cm}=0.9V$)

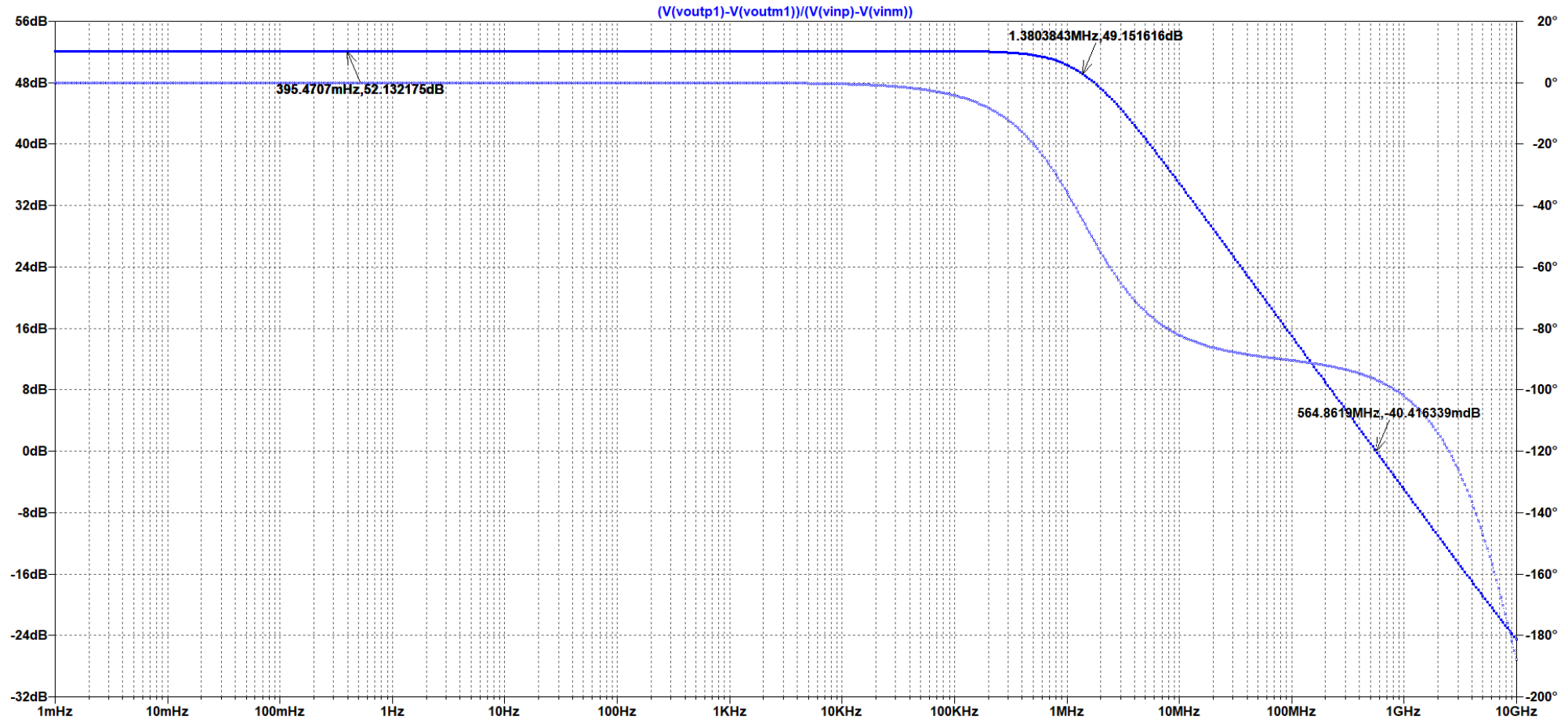


AC Analysis

 

CMFB



Principle of CMFB

 - Common Mode Feedback to correct for V_{cm} because of variation in PMOS and NMOS current pairs
- Compare the Common mode voltage to reference voltage
- Output signal of CMFB Stage can be fed back
- Providing it on gate terminal helps in controlling V_{gs} and hence, current through it.



Detection of Common mode voltage

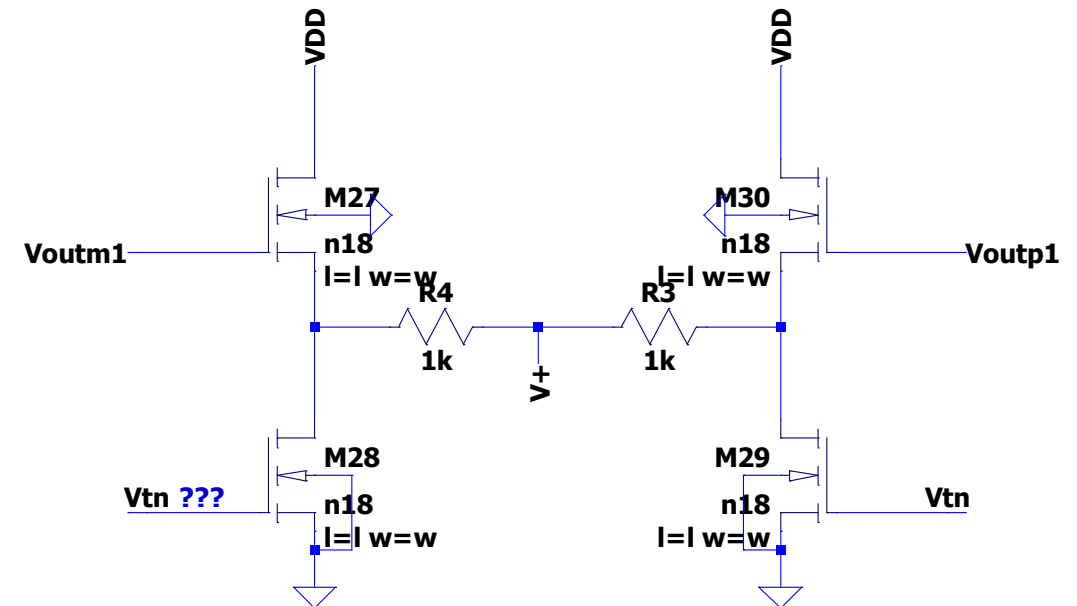 - Sensed by simple resistor
- But direct resistor comes parallel to R_{out}
- Results in low gain
- Require high value of Resistor
- Solution is to use buffer stage
- Followed by low value resistor to detect the output V_{CM}




Source Follower

Benefits:

- Very high input impedance

Price:


 
- Voltage(V_{GS}) drop across the M2 transistor
- Reference voltage = $V_{CMref} - V_{GS}$




- $V_{CMref} = 0.9V$
- $V_{GS} = 0.593V \approx 0.6V$

Correction for Common Mode voltage

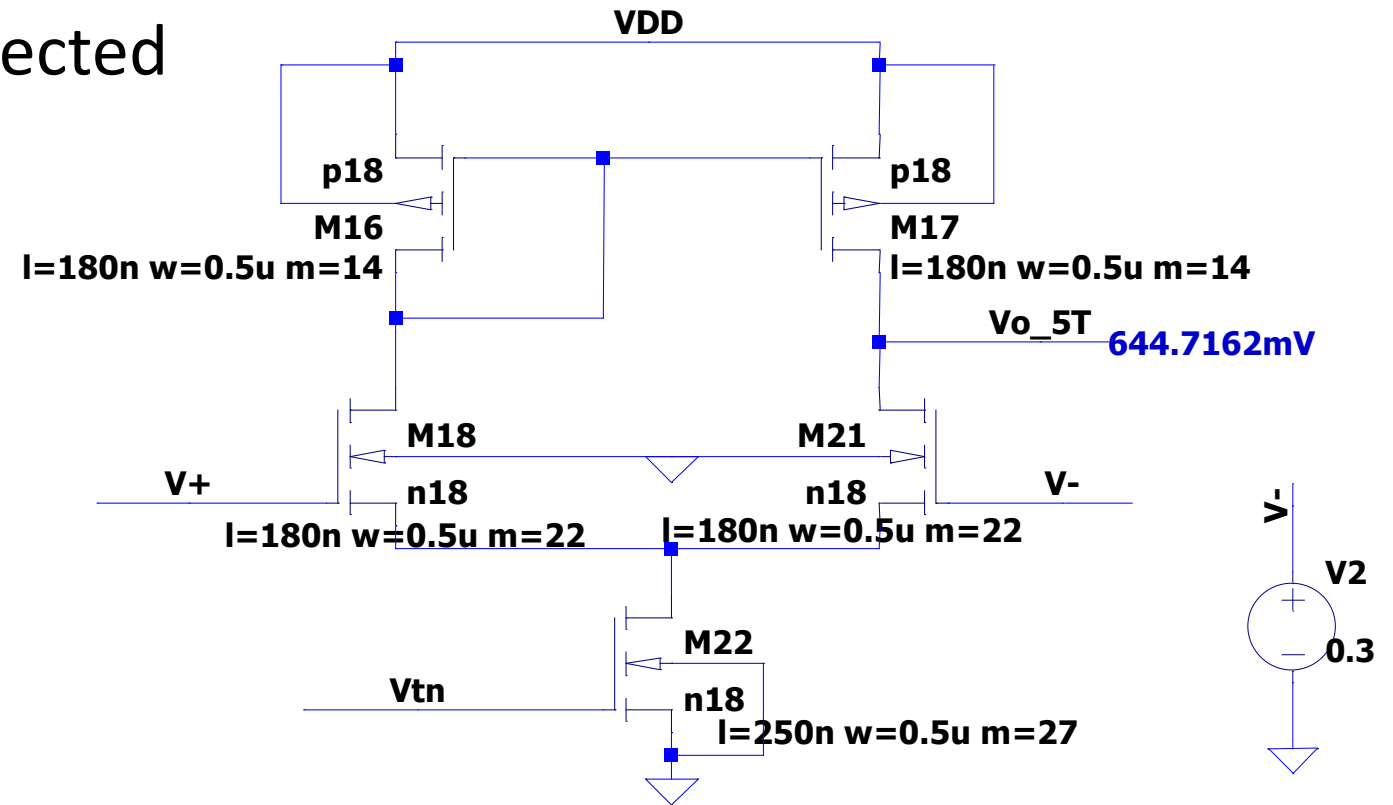 - Common Mode voltage detected
- CMFB stage: 5T OTA
- Output: Vo_5T
- Reference voltage : (V-)
 - $(V-) = V_{CMref} - V_{GS} = 0.3$




DC Analysis

 


- Input CM Voltage
 - Sweep from -0.5V to 2.5V
- Output DC Voltage
 - Not much Variation.
- Rail to Rail working capability
 - Input CM voltage
 - Full Range

DC Analysis

 - Input CM Voltage
 - Sweep from -0.5V to 2.5V
- Output CM Voltage
 - Range: 0.4V to 1.4V
- Output of CMFB Stage
 - Range: 0.4V to 1.4V
 - Similar behavior




AC Analysis

 


Folded cascode with CMFB

Transient Analysis

 - To simulate current disturbance:
extra current source used.
- Current sources in parallel with
the MOSFET
- Current source: Pulse input




Results

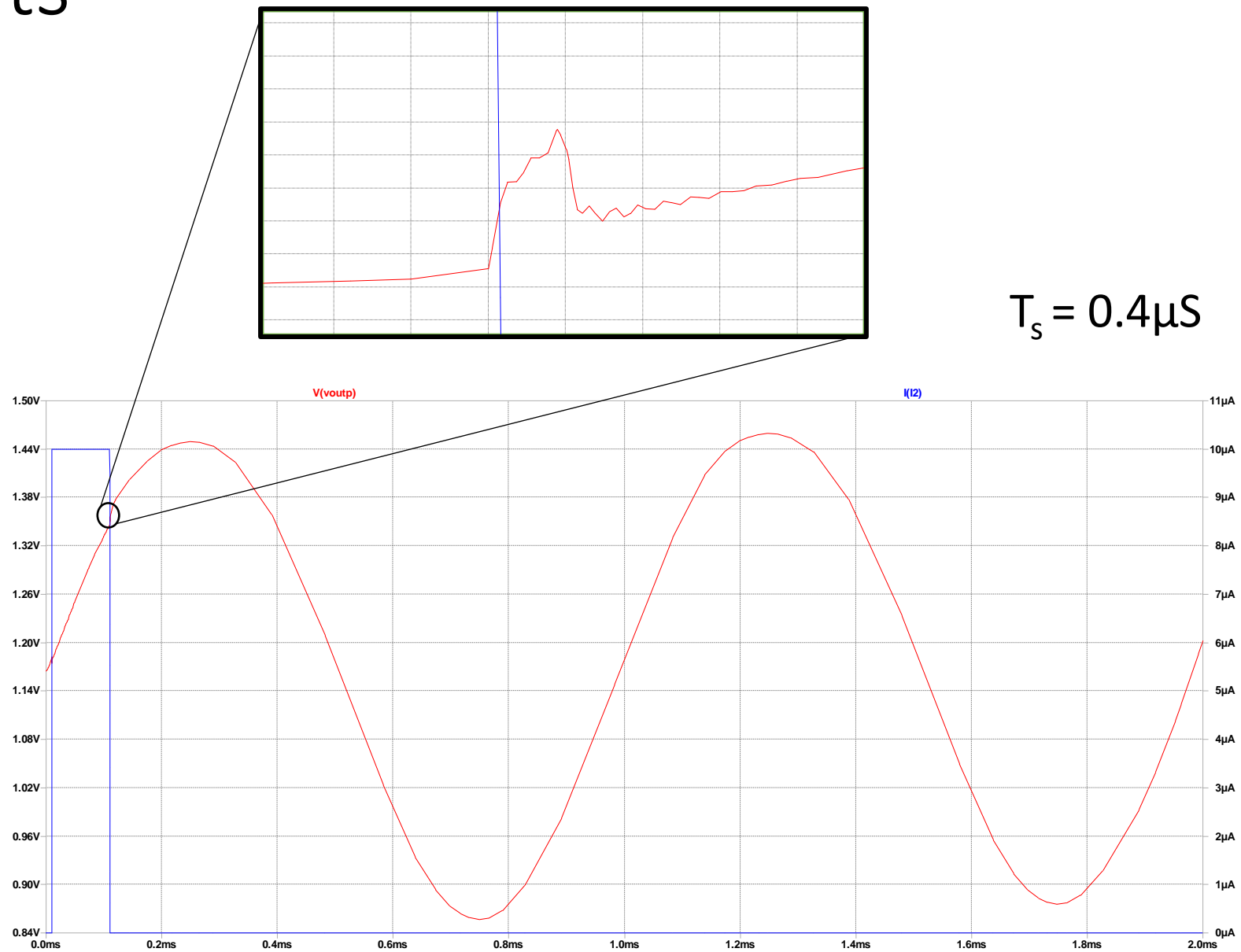

Transient Voltage analysis

$T_s = 0.4\mu S$


 


2nd Stage

Design Budgeting


- Common source amplifier
- Design parameters:
 - V_{gs} (for second stage)
 - $V_{gs} = V_{DD} - V_{CMRef} = 1.8V - 0.9V = 0.9V$
 - $A_{v,req}$ (Required gain) $\sim 25dB = 17.78$
- Calculation:
 - $A_{v,req} = 17.78 = g_m * R_{out}$
 - $(2.22m) * (8k\Omega) = 17.78$
 - $R_{out} \sim 8k\Omega$
 - $g_m \approx 2.22mS$

PMOS Characterization

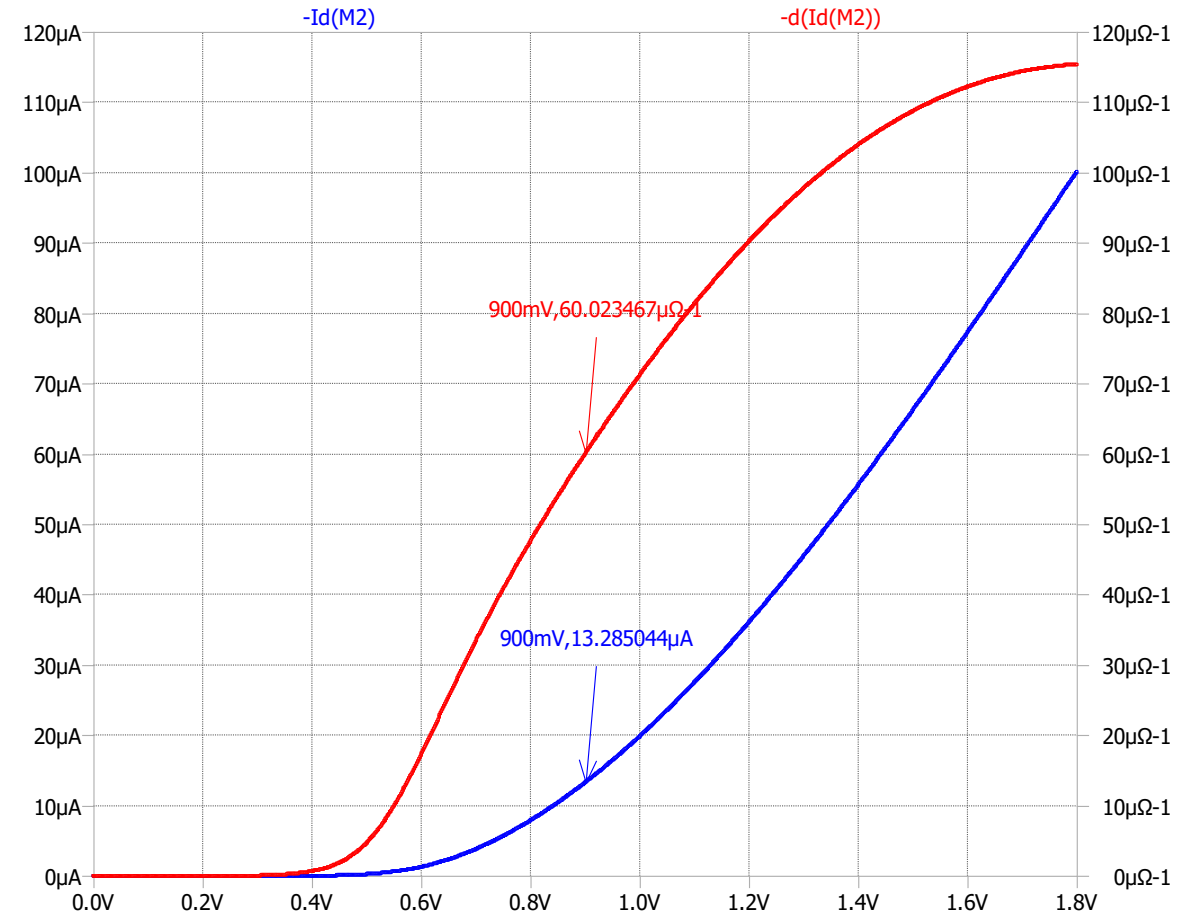 

- Scaling factor(multipliers) = $\frac{2.22mS}{60.023467\mu S} = 36.98 \approx 37$

2nd Stage Design

 

2nd Stage Circuit


Name:	m6	m25	m23	m17	m16
Model:	n18	p18	p18	p18	p18
Id:	1.54e-04	-4.30e-04	-4.30e-04	-2.85e-07	-2.08e-07
Vgs:	6.76e-01	-8.98e-01	-8.98e-01	-3.94e-01	-3.94e-01
Vds:	7.02e-01	-6.57e-01	-6.57e-01	-1.16e+00	-3.94e-01
Vbs:	-2.01e-01	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Vth:	5.19e-01	-5.14e-01	-5.14e-01	-5.11e-01	-5.16e-01
Vdsat:	1.54e-01	-3.00e-01	-3.00e-01	-3.91e-02	-3.89e-02
Gm:	1.50e-03	2.04e-03	2.04e-03	6.47e-06	4.75e-06
Gds:	4.15e-05	9.37e-05	9.37e-05	1.09e-07	9.38e-08

Operating Point

Simulation Results

- $g_m = 2.04\text{mS}$
- $R_{\text{out}} = 10.672\text{k}\Omega$
- $\text{Gain}(A_v) = 23.32\text{dB}$
- Cut-off Frequency(f_c)
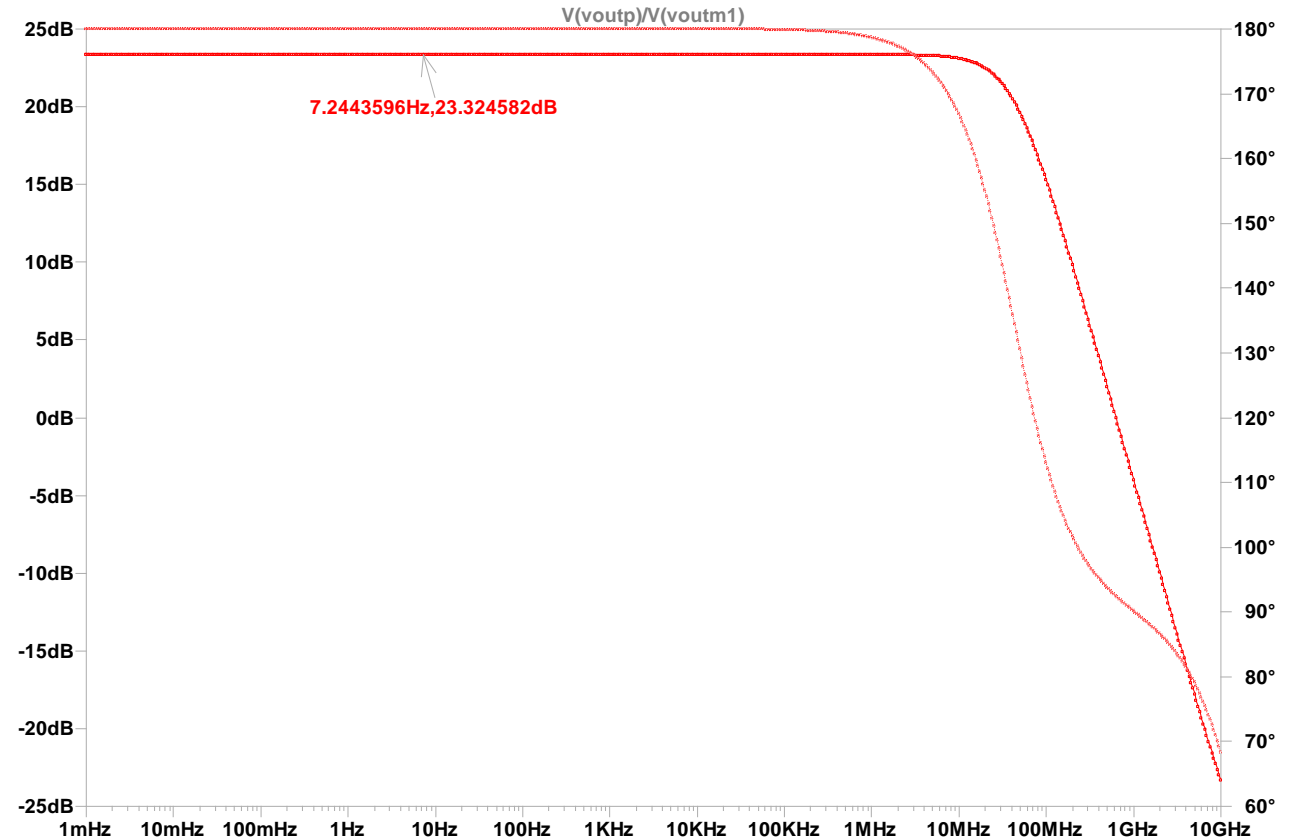
$$\frac{1}{2\pi R_{\text{out}} C_{\text{out}}} = 29.83\text{MHz}$$



Gain Plot

Phase Compensation(Miller compensation)


- Resistor Calculation:

$$R_z > \frac{1}{g_m}$$



$$\frac{1}{g_m} = 490.196\Omega$$

Taking $R_z = 500\Omega$

 - Taking arbitrary value for capacitor $c_c = 500\text{fF}$




Circuit Design

 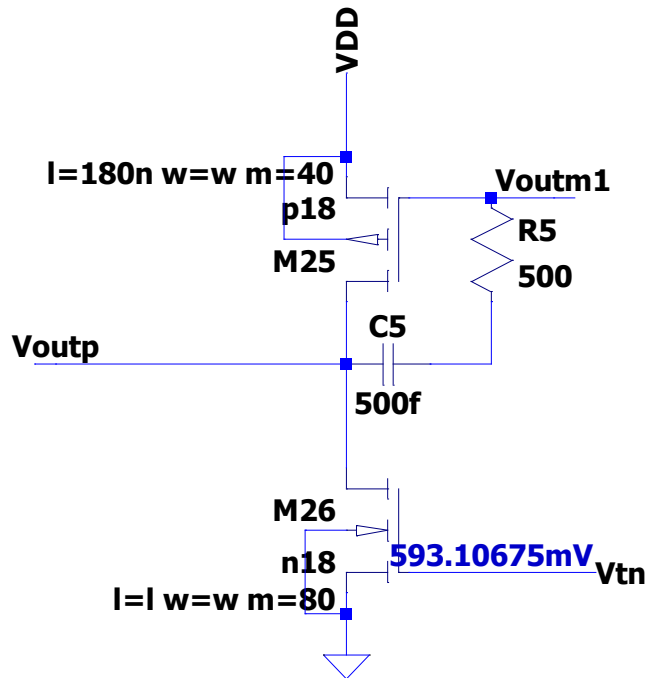

2nd Stage with miller compensation(between 1st and 2nd stage)


Simulation result

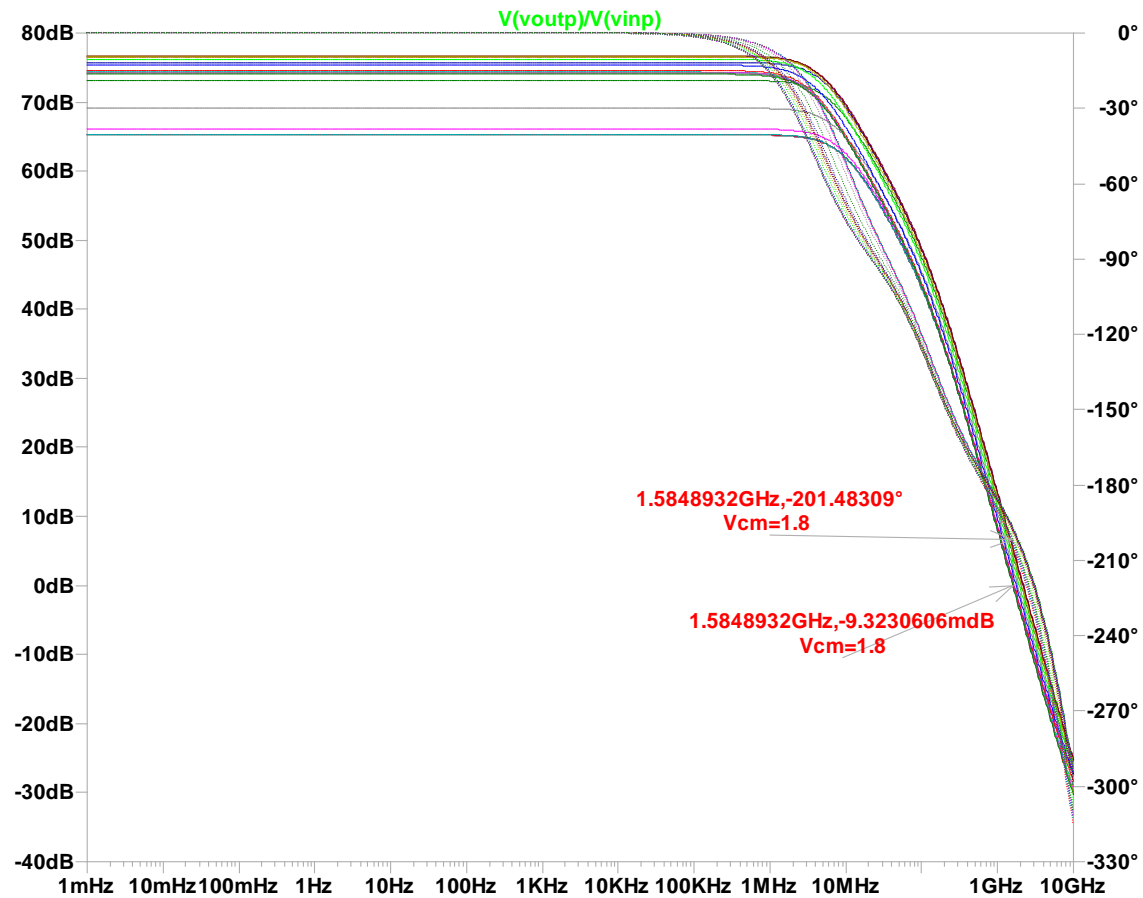

Without Miller Compensation

Gain Cross-over frequency = 1.584GHz

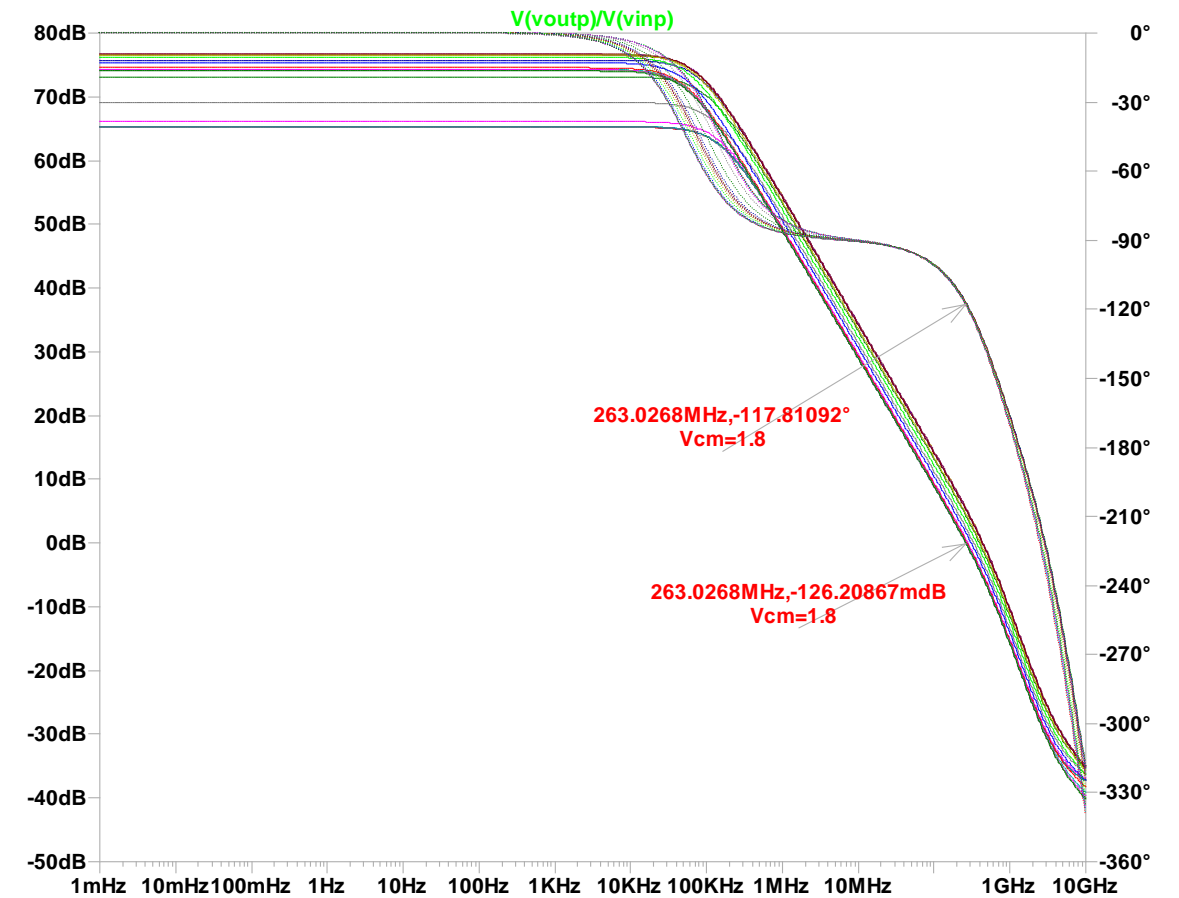Phase margin = $-201.48 + 180 = -21.48$ (Unstable)




With Miller Compensation

Gain Cross-over frequency = 263.02 MHz

Phase margin = $-117.81 + 180 = 62.19$ (stable)


Results

DC Analysis

 


- Input CM Voltage
 - Sweep from -0.5V to 2.5V
- Output DC Voltage of Stage-1
 - Range: 0.4V to 1.4V
 - Not much variation
- Output DC Voltage of Stage-2 (Final O/P)
 - Range: 0.4V to 1.4V
 - Not much variation
- Rail to Rail working capability
 - Input CM voltage – Full Range


AC Analysis ($V_{CM} = 0.9V$)

 

AC Analysis (V_{CM} sweep)

 

AC Analysis (V_{CM} sweep)

 

Results & Conclusion

- Gain
 - 65.3 dB to 76.63 dB
- BW
 - 156.055 kHz to 77.16 kHz
- UGF
 - 263 MHz to 436.5 MHz
 - $UGF > 100 \text{ MHz}$
- Phase margin
 - 48° to 63°
- Power Consumption (Overall)
 - $1.8 * 1.37 \text{ m} = 2.467 \text{ mW}$
- Power Consumption (w/o bias)
 - $1.8 * 1.33 \text{ m} = 2.39 \text{ mW}$
- Input common mode range
 - Rail-to-Rail
- CMFB
 - Working

Improvements

- Rail-to-Rail input capabilities in stage-1 (folded cascode)
- Gm Calibration
- Overall Gain Improvements

References

- Design of Analog CMOS Integrated Circuits, B. Razavi
- ECEN474/704: (Analog) VLSI Circuit Design (Spring 2018), Sam Palermo
Analog & Mixed-Signal Center, Texas A&M University
 - Lecture 15: Fully Differential Amplifiers & CMFB
 - Lecture 17: Fully Differential Amplifiers & CMFB
- Lecture notes

THANK YOU!